 


Day 06

Half Subtractor & Full Subtractor in Verilog

1) HALF SUBTRACTOR



Inputs		Outputs	
A	B	Difference	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0


Verilog Code

```
1 module half_subtractor(a, b,diff, borrow);
2     input a, b;
3     output diff, borrow;|
4
5     assign diff = a ^ b;
6     assign borrow = ~a & b;
7
8 endmodule
9
```


Testbench Code

```
1 module half_subtractor_tb;
2     reg a, b;
3     wire diff, borrow;
4     half_subtractor DUT (a,b,diff,borrow);
5
6     initial begin
7         $monitor($time,"a=%b b=%b => diff=%b borrow=%b", a, b, diff, borrow);
8         a = 0; b = 0; #10;
9         a = 0; b = 1; #10;
10        a = 1; b = 0; #10;
11        a = 1; b = 1; #10;
12        $finish;
13    end
14 endmodule
15
```


Waveform

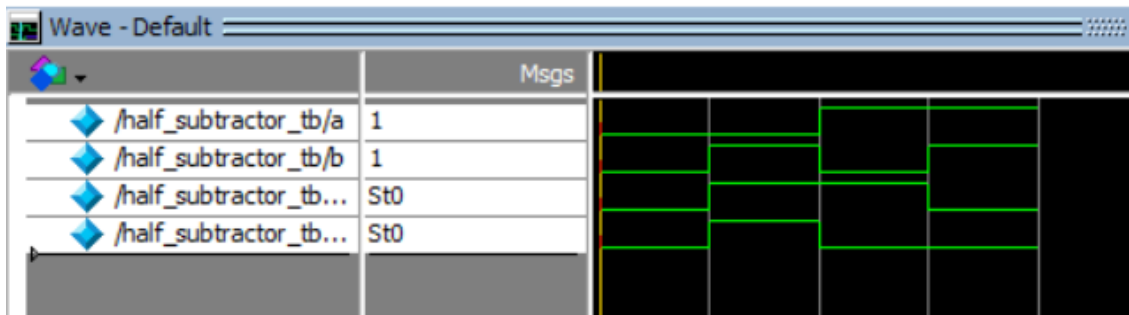

Schematic

 

2) FULL SUBTRACTOR

 

A	B	B _{in}	D	B _{out}
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


Verilog Code

```
1 module full_subtractor(a, b, bin, diff, borrow);
2     input a, b, bin;
3     output diff, borrow;
4     assign diff = a ^ b ^ bin;
5     assign borrow = (~a & bin) | (~a & b) | (b & bin);
6 endmodule
7
```


Testbench Code

```
1 module full_subtractor_tb;
2     reg a, b, bin;
3     wire diff, borrow;
4     full_subtractor DUT (a,b,bin,diff,borrow);
5
6     initial begin
7         $monitor("a=%b b=%b bin=%b | diff=%b borrow=%b", a, b, bin, diff, borrow);
8         repeat(8) begin
9             {a, b, bin} = $random;
10            #10;
11        end
12        $finish;
13    end
14 endmodule
```

Waveform

 

Schematic

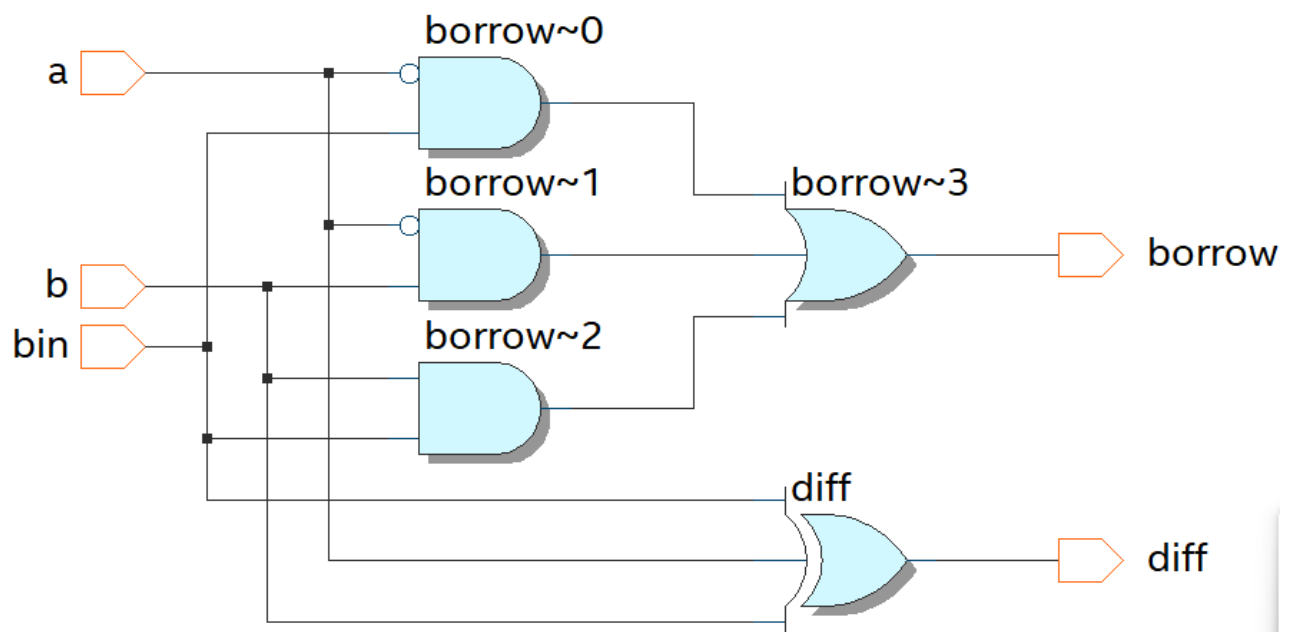

EDA Tools Used

- IntelQuartusPrime
- ModelSim

© 2025 Satyam Nishad | 100 Days RTL Coding Challenge